

1246432168421

University of Tripoli - Faculty of Engineering  
Electrical & Electronic Engineering Department

EE463

Final Exam Time: 2 hr Spring 2017

3/2/2018

Q1) Temperature sensor sensitivity is  $4\Omega/^\circ C$ , in the range ( $\pm 25^\circ C$ ) and its value at  $0^\circ C$  is  $280\Omega$ . Using Wheatstone bridge convert its range to volt, and send its value using (4mA -20mA transmitter) and prepare it for 8bit ADC with voltage reference 0-5Vref.

a) What is the digital output of ADC at the temperature  $-2^\circ C$ . [12 pts]

Q2) Accelerometer sensor sensitivity is  $0.33mA/g$ , used for measuring Acceleration in the range ( $\pm 20g$ ). Design signal condition circuits for bipolar (8 bit) ADC with voltage reference  $\pm 4V$ .

a) What is the digital output of ADC at the acceleration is  $-3g$ . [12]

b) What is the acceleration when the digital output is 06H. [12 pts]

Q3) Design the signal conditioning circuits to connect the sensor to 10 bit ADC with voltage reference (0-5V), where: sensor output range ( $-150 - +150 mV$ ) with frequency 15Hz. Noise signal 20mV with frequency 150Hz, and design filter that Attenuate the noise signal to 25%, and taking in account the effect of the filter on the sensor signal. [10 pts]

$V_o = V_i \cdot 0.25$

Q4) Using Thermocouple sensor Type J with  $0^\circ C$  reference, find the value of its output at  $32^\circ C$ . Design circuit to operate cooler if the temperature is more than  $32^\circ C$ , and using RTD with the following table using linear approximation of resistance versus temperature find the value of the RTD at  $13^\circ C$  and design circuit operate heater if the temperature is less than  $13^\circ C$ . [12 pts]

Temperature ( $^\circ C$ )	0	5	10	15	20
Resistance ( $\Omega$ )	107.6	109.1	110.2	111.1	111.7

RTD =  $110.2\Omega$   
 $V_m = 1.936mV$

Q5) What is the sampling and sample and hold and aliasing and oversampling (Draw as you can) [4 pts]

Good Luck (Zeyad)

Q4) Thermocouple Sensor Type J with 0°C ref  
 O/p if  $T = 32^\circ\text{C}$  to operate cooler ~~at  $32^\circ\text{C}$~~   $T > 32^\circ\text{C}$   
 using RTD with Table using linear approximation  
 RTD ?) at  $13^\circ\text{C}$   
 - operate heater if  $T < 13^\circ\text{C}$


T	0	5	10	15	20
R	107	109.4	110.2	111.1	111.5

$V_L = 1.54 \text{ mV}$       $T_L = 30^\circ$   
 $V_H = 1.80 \text{ mV}$       $T_H = 35^\circ$   
 $T_m = 32^\circ\text{C}$

$$V_m = V_L + \left[ \frac{V_H - V_L}{T_H - T_L} \right] (T_m - T_L)$$

$$= 1.54 + \left[ \frac{1.80 - 1.54}{35 - 30} \right] (32 - 30)$$

$$V_m = 1.644$$

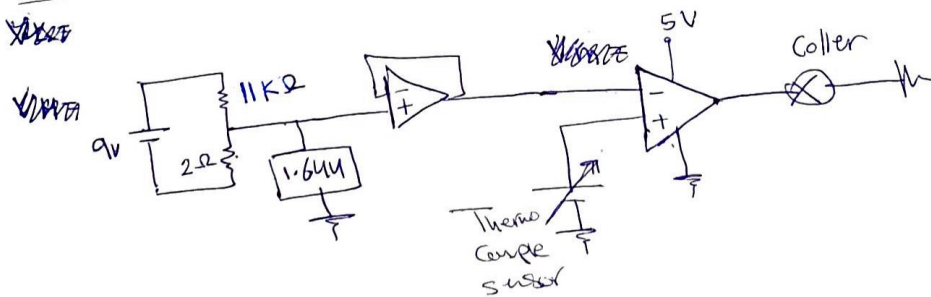

$$Q \times \frac{R}{11k\Omega + R} = 1.644 \text{ mV}$$

$$R = 2 \Omega \#$$

$$T_1 = 0, R_1 = 107$$

$$T_0 = 10, R_0 = 110.2$$

$$T_2 = 20, R_2 = 111.5$$

$$\alpha_0 = \frac{1}{R(T_0)} \times \frac{R_2 - R_1}{T_2 - T_1} = \frac{1}{110.2} \times \frac{111.5 - 107}{20 - 0} = 2.041 \times 10^{-3}$$

$$R(T) = R(T_0) (1 + \alpha_0 \Delta T)$$

$$= 110.2 [1 + 2.041(13 - 10)]$$

$$= 110.87 \Omega$$

